


Aim: To study the working of Schmitt trigger, Multivibrators and precision rectifiers.

Software used: LTspice


Schmitt trigger:

(a) When V_a is connected to ground:


Circuit:

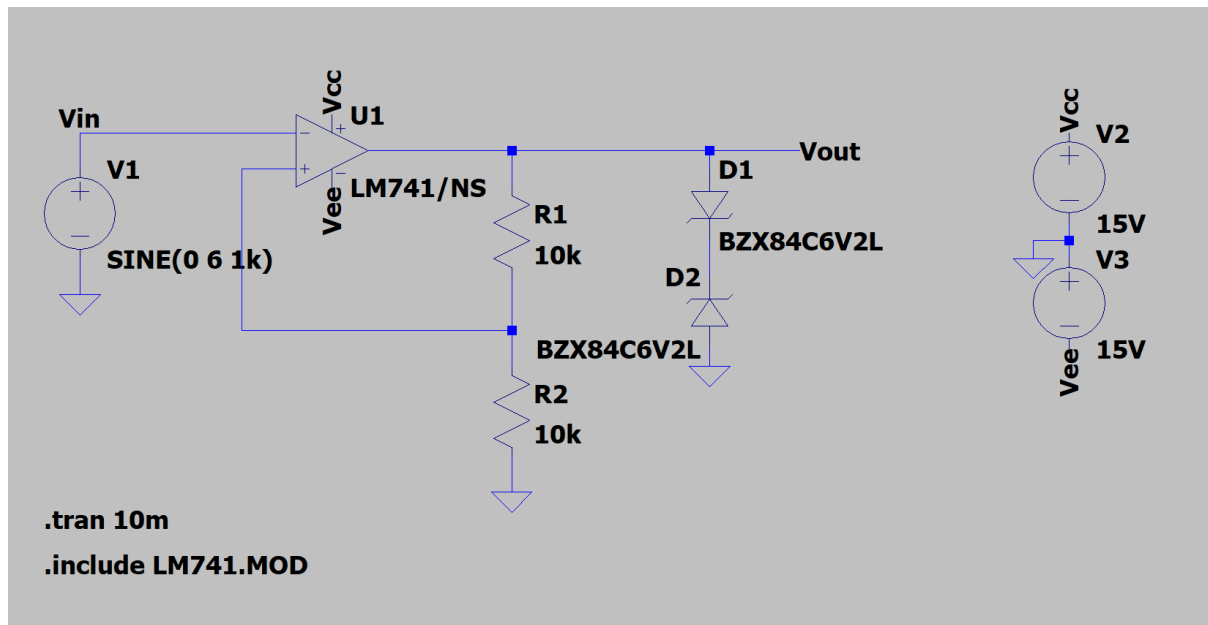

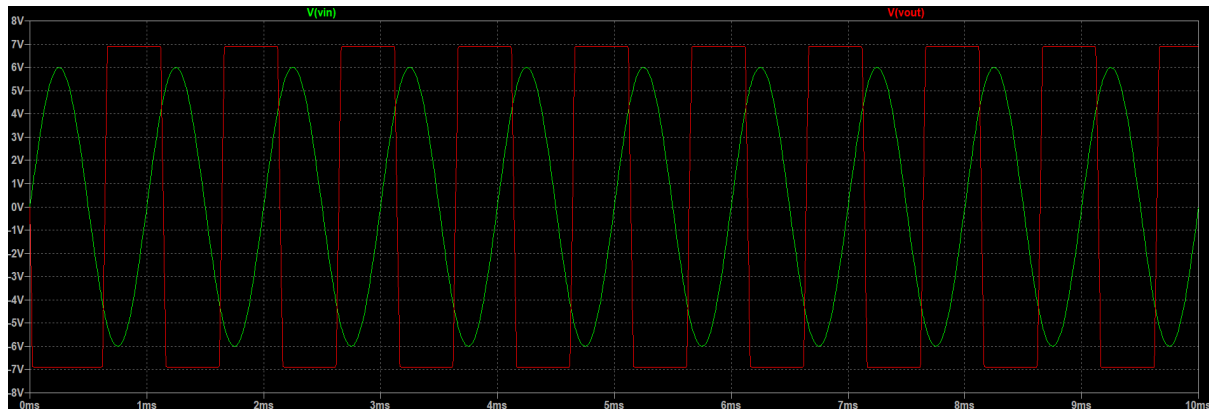Output waveform on scope when 6V, 1kHz sine wave is applied:




Input and output waveforms in X-Y mode:

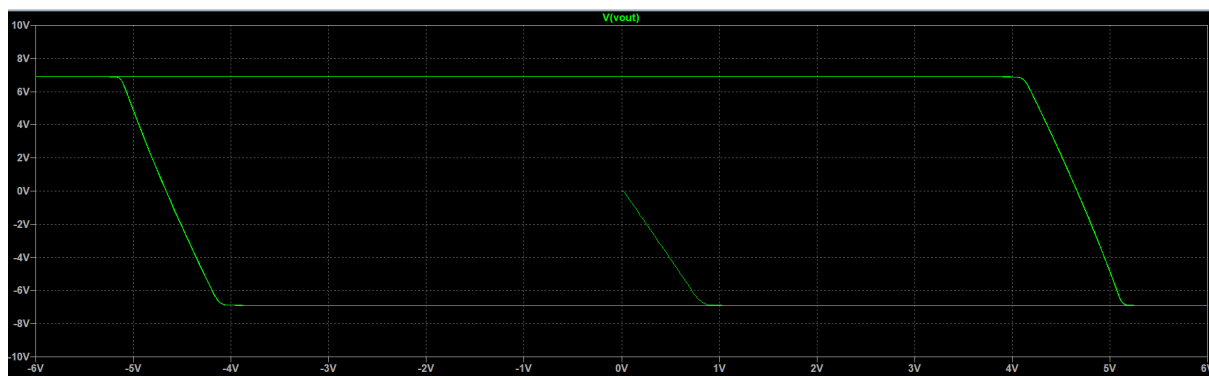


(b) When V_a is connected to 3V:


Circuit:

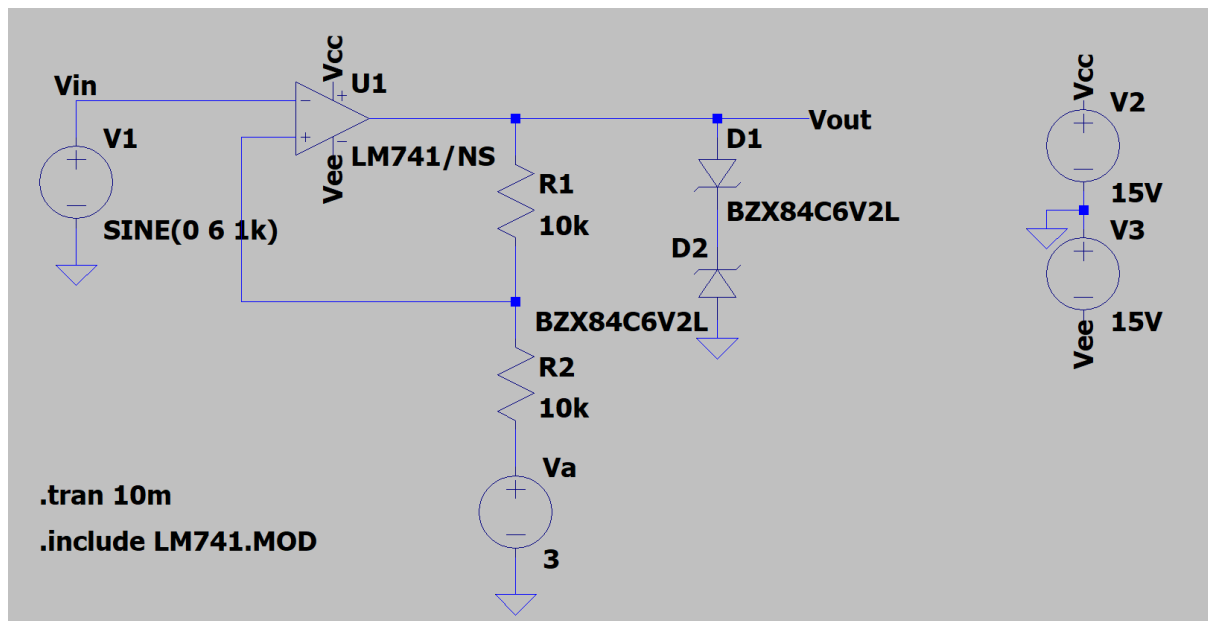

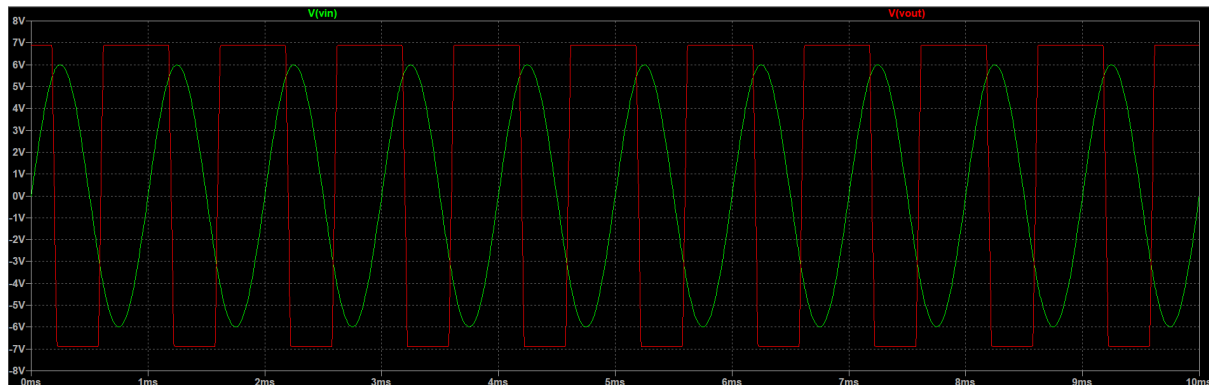Output waveform on scope when 6V, 1kHz sine wave is applied:




Input and output waveforms in X-Y mode:

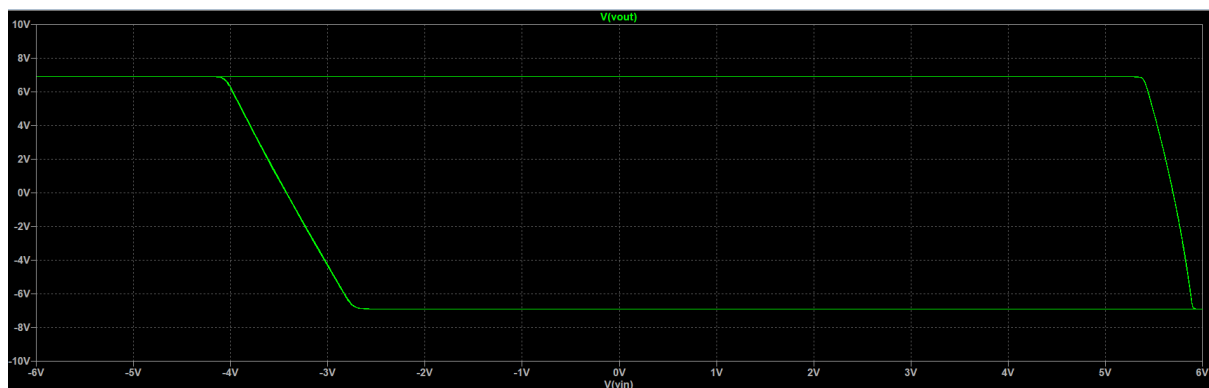


Astable multivibrator:


Circuit:

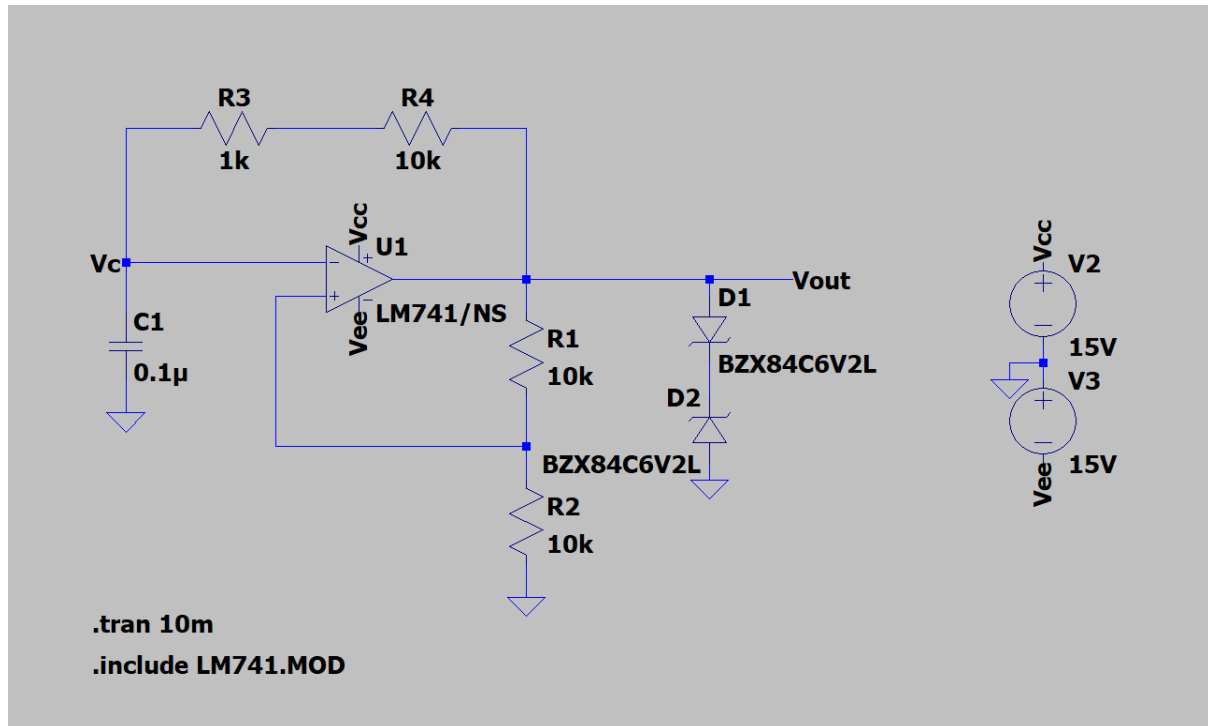

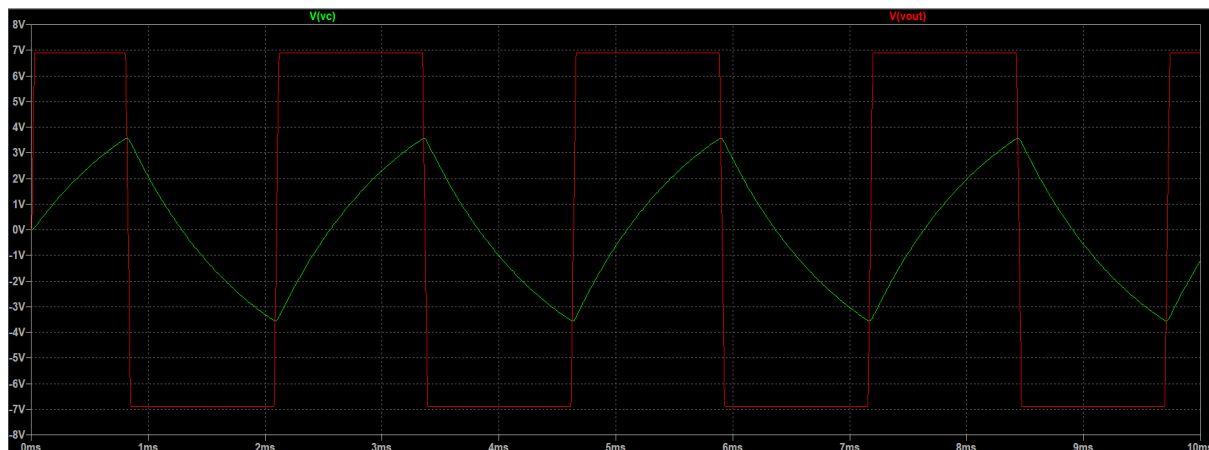Output voltage (red) and voltage across capacitor (green) observed on scope:



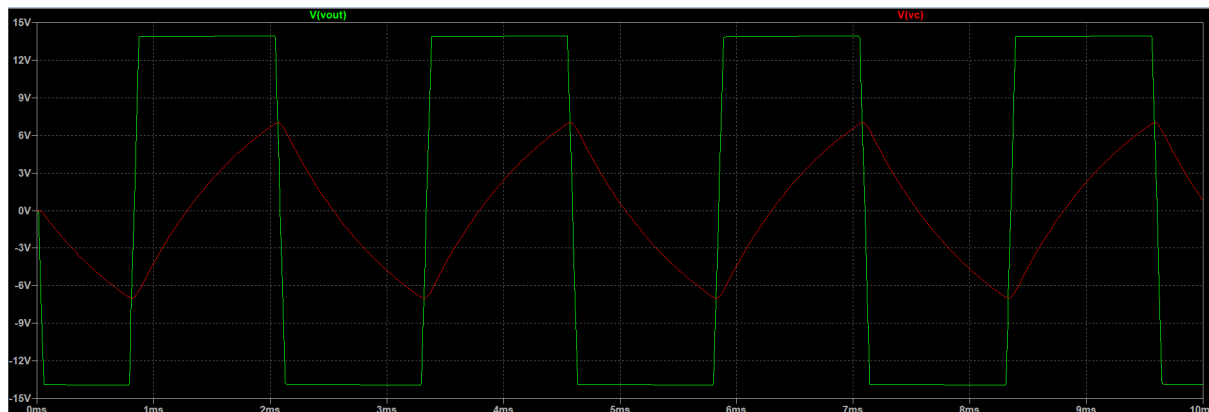Observed waveforms after disconnecting the zener diodes:




No, The frequency of waveforms didn't change because the time period of the output voltage and voltage across capacitor is given by

$$T = 2RC \ln \left(1 + \frac{2R_2}{R_1} \right)$$


Monostable multivibrator:

Circuit:

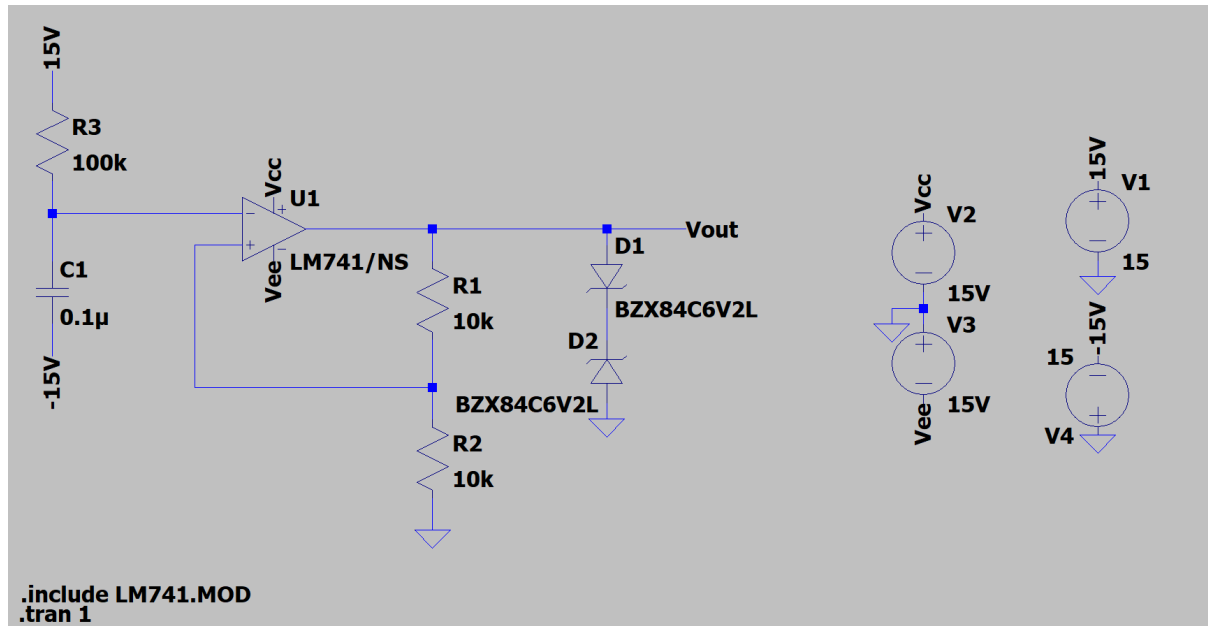


*The circuit above is the given circuit in the lab manual from which I am not getting the correct output.

Circuit explained in lab:

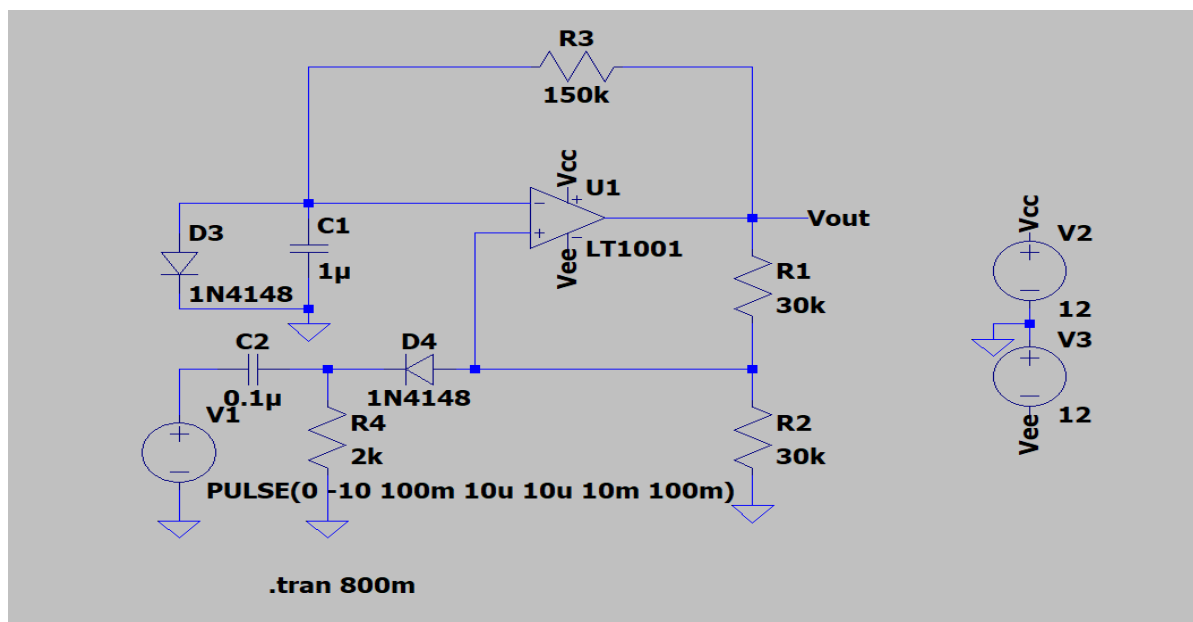

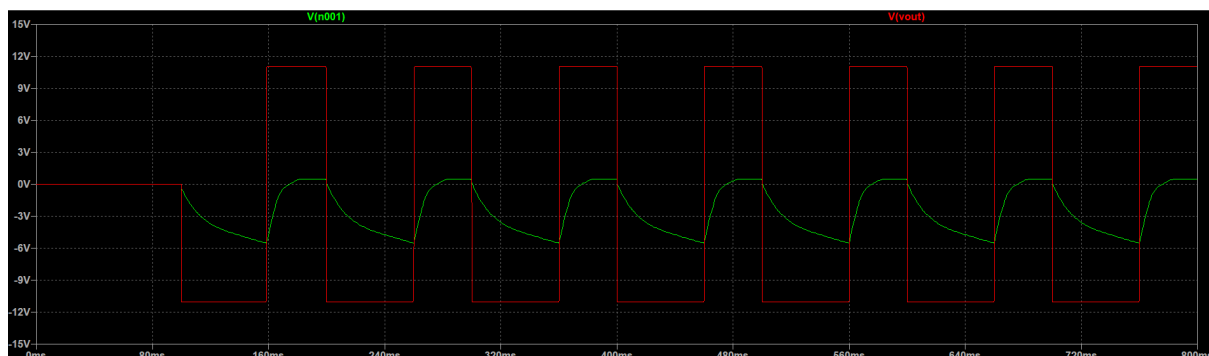
Output voltage and Voltage at the inverting opamp's terminal:




Half wave Rectifier:

A) Positive Rectifier:

Circuit:

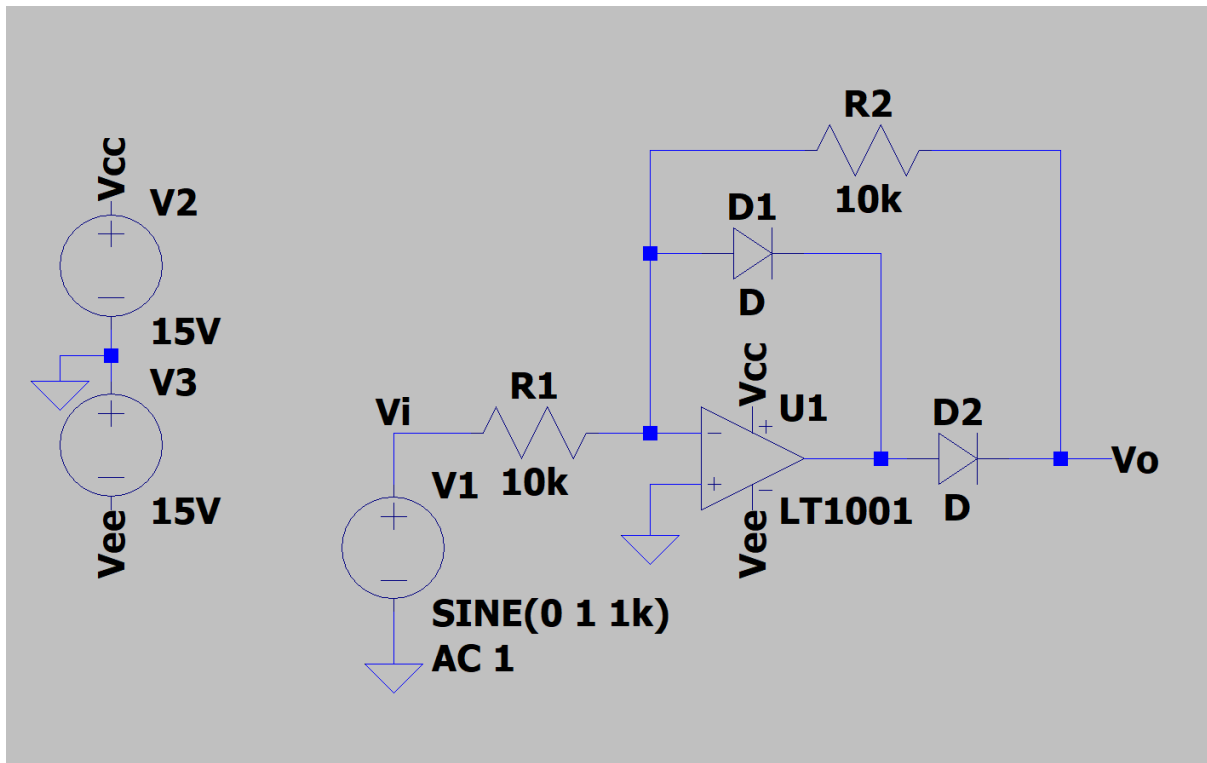

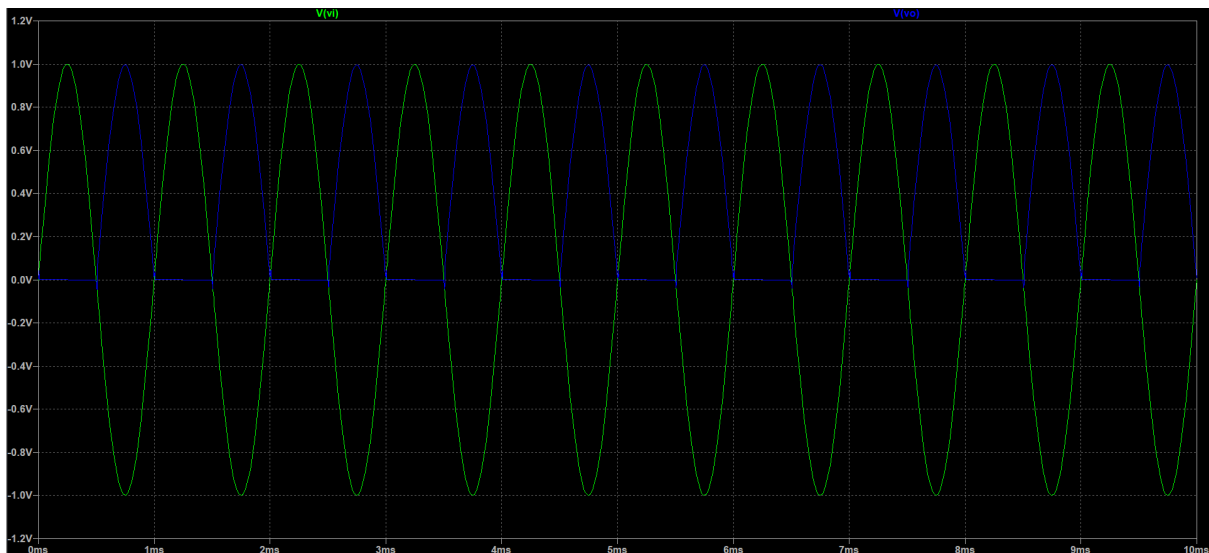Input and Output voltage waveforms on scope when 1V, 1kHz sine wave is applied:




Transfer characteristics:




B) Negative Rectifier:


Circuit:

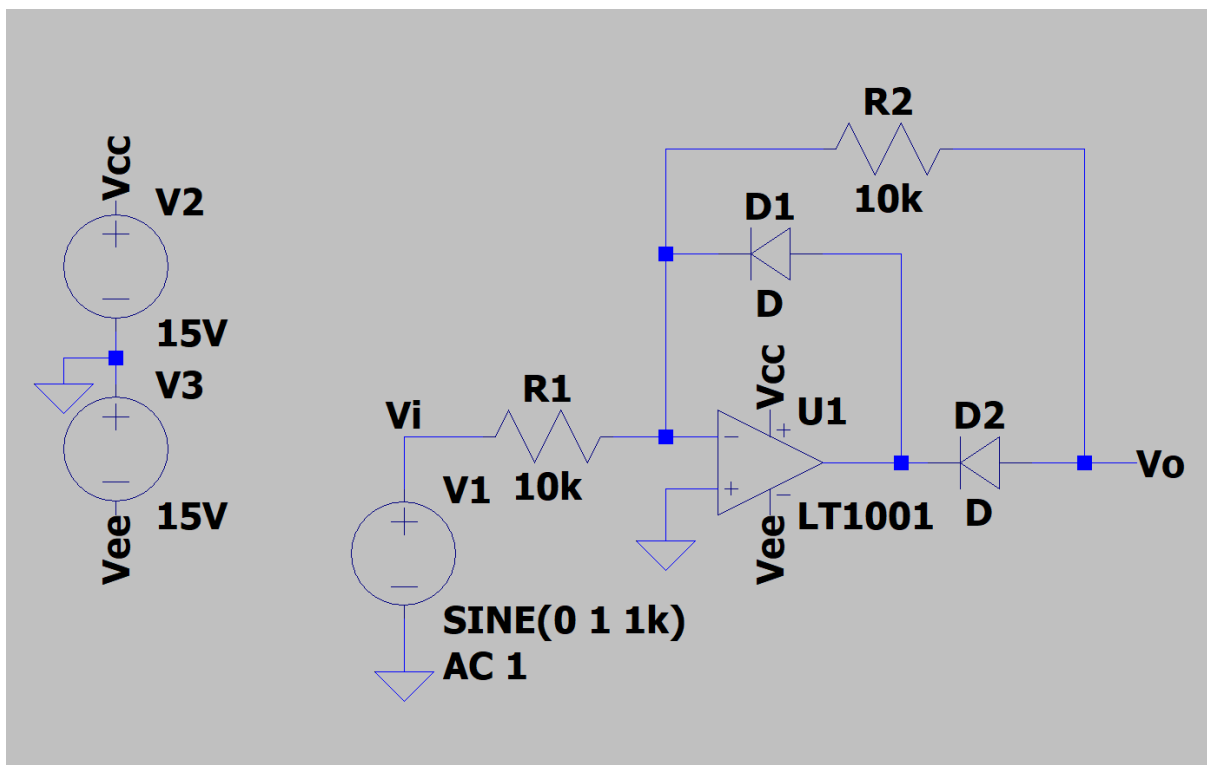

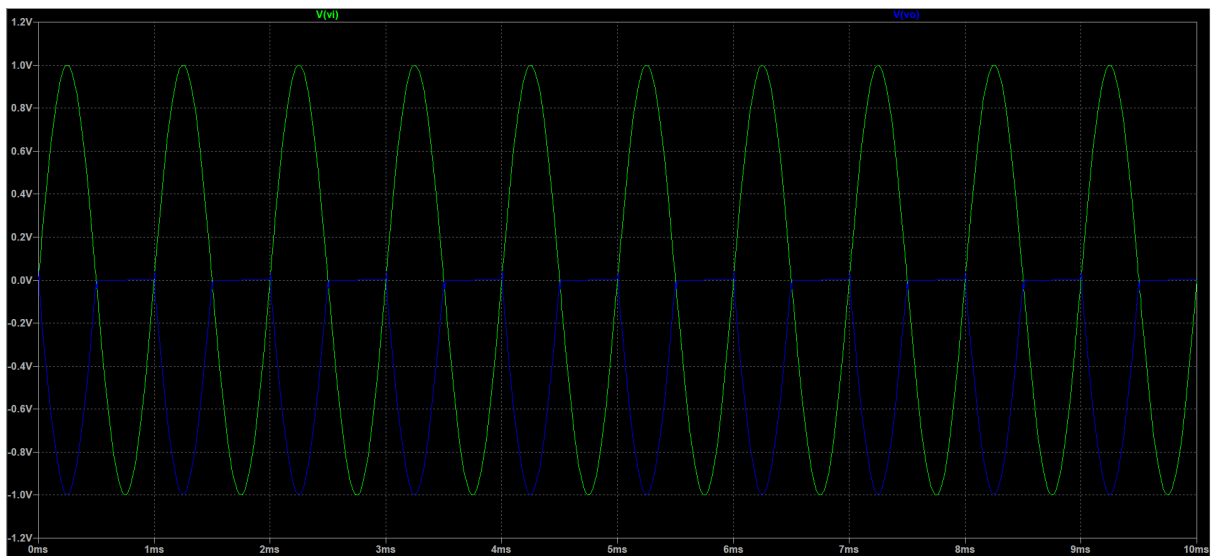Input and Output voltage waveforms on scope when 1V, 1kHz sine wave is applied:




Transfer characteristics:

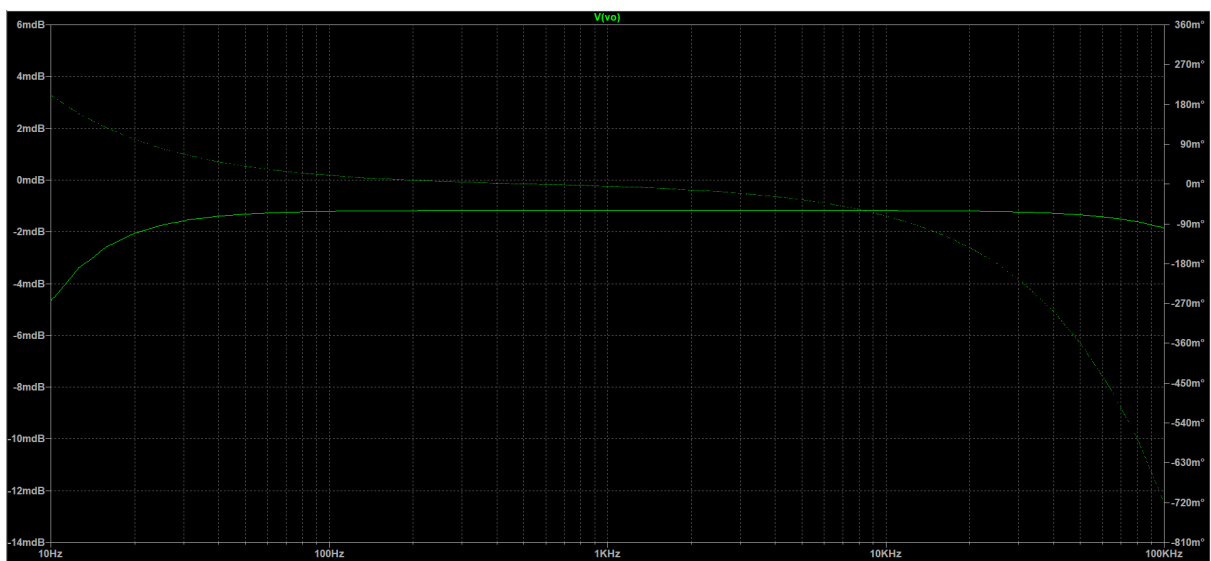


Full wave Rectifier:

A) Positive Rectifier:


Circuit:

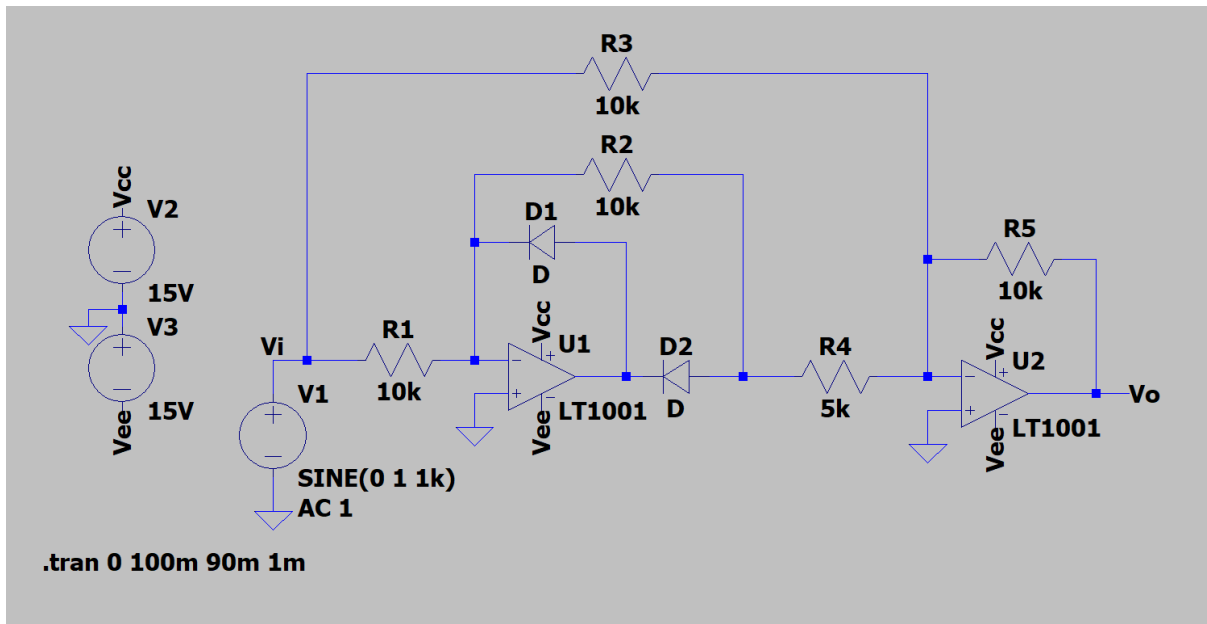

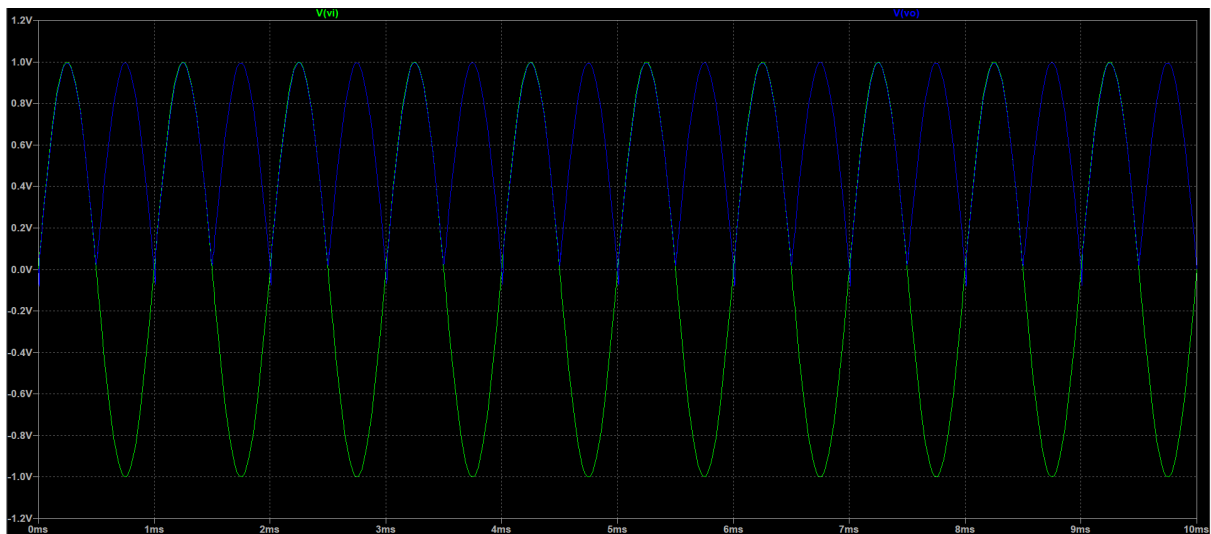Input and Output voltage waveforms on scope when 1V, 1kHz sine wave is applied:




Transfer characteristics:

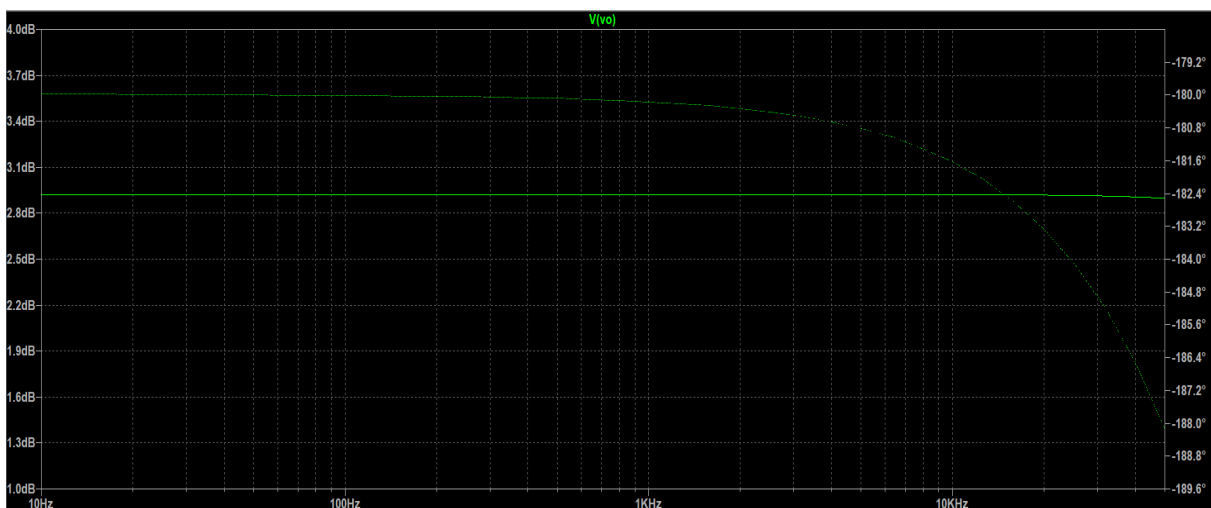


B) Negative Rectifier:

Circuit:

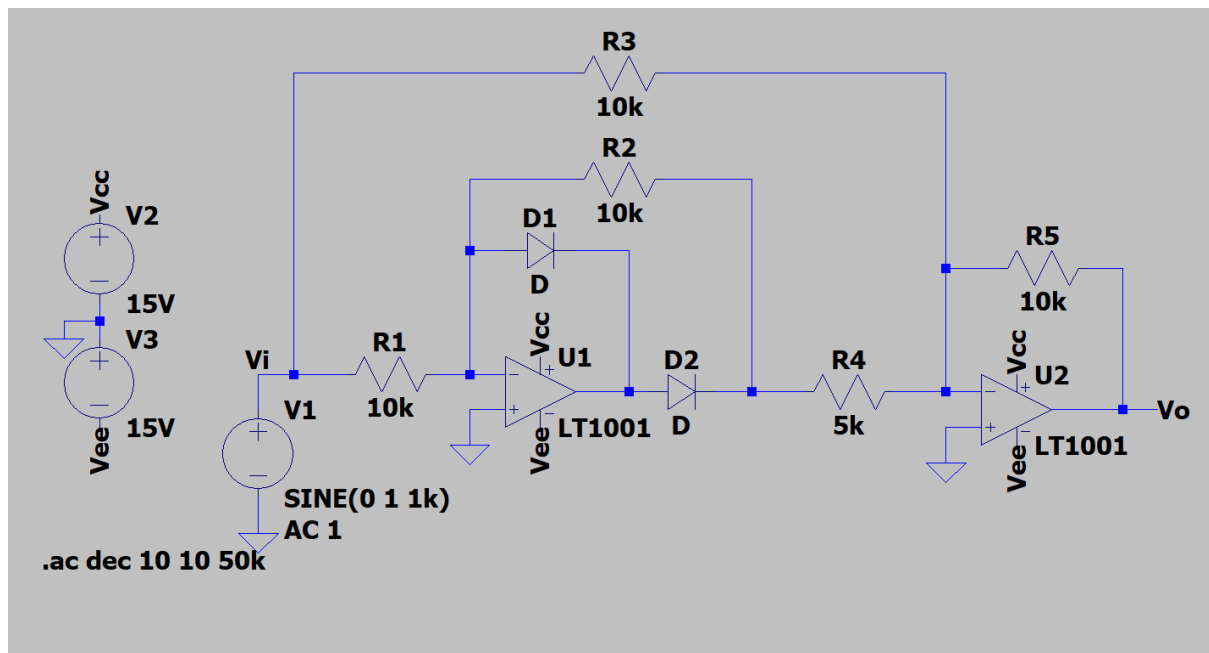

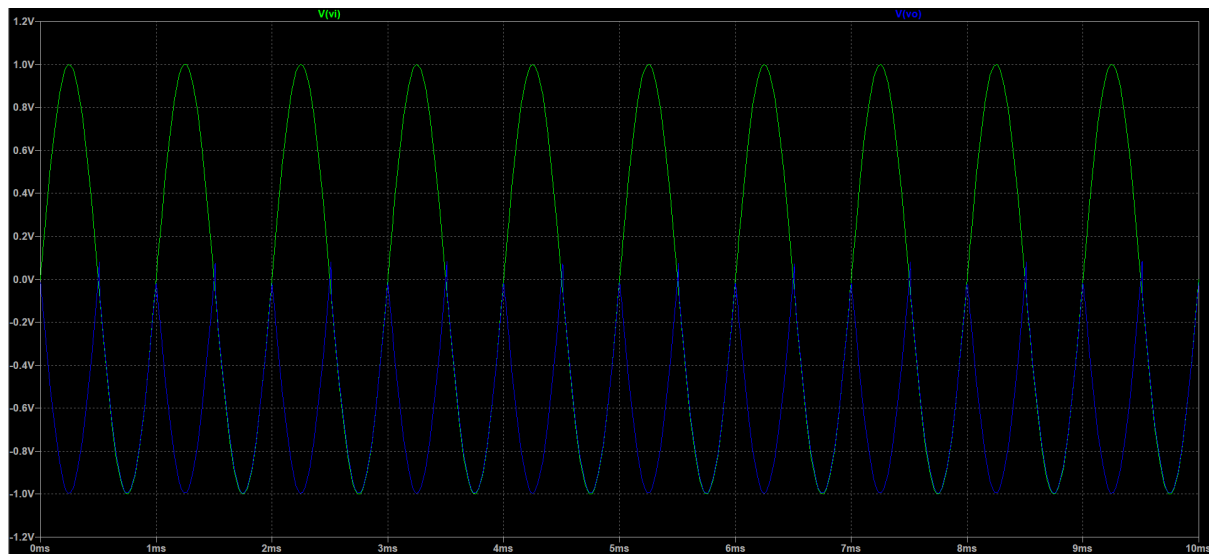Input and Output voltage waveforms on scope when 1V, 1kHz sine wave is applied:



Transfer characteristics:

