

Aim: To study the working of Wien bridge oscillator, log and antilog amplifiers.

Software used: LTspice

Wein bridge oscillator:


(a) Take $C = 0.1 \mu\text{F}$ and calculate R so as to get a frequency of 1 kHz for the output V_o .

$$f = 1/(2\pi RC)$$


$$R = 1/(2\pi \cdot 1000 \cdot 0.1 \cdot 10^{-6})$$

$$R = 1.59 \text{ kohm}$$

Circuit:

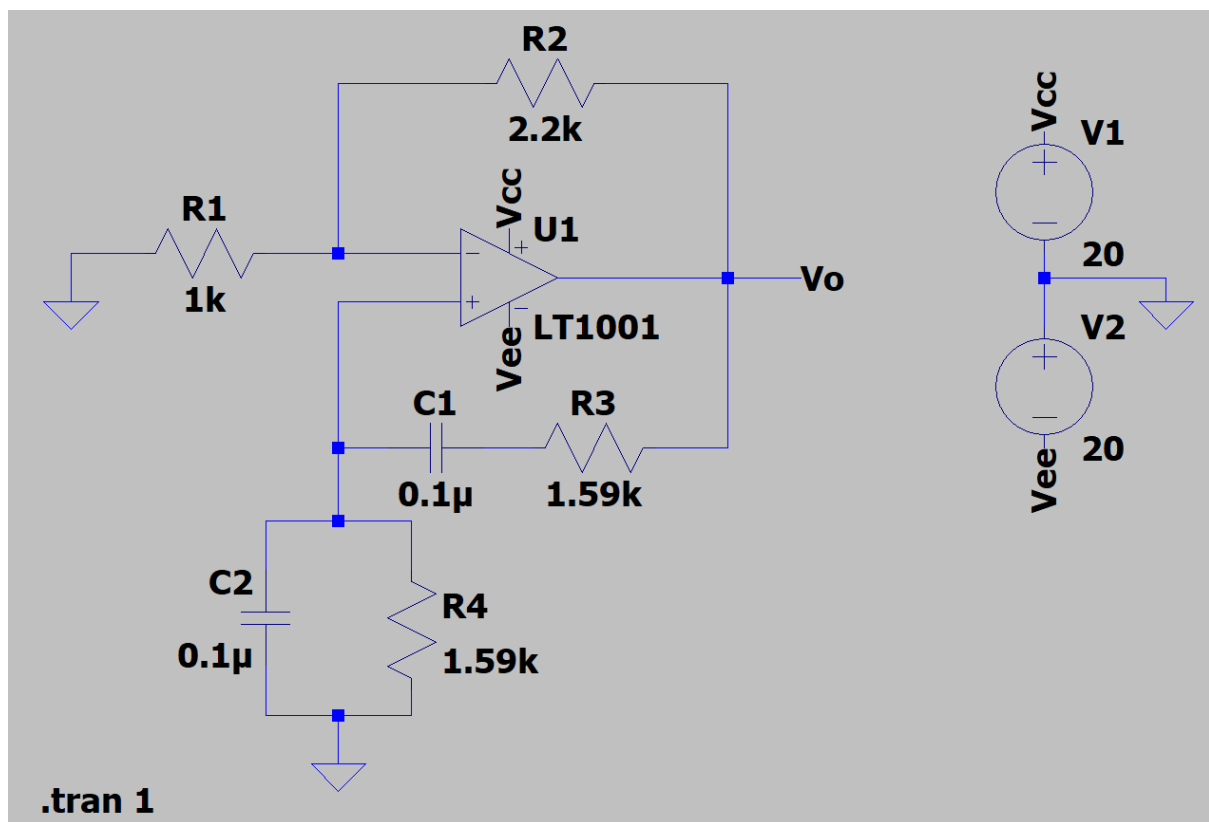


Output waveform on scope:

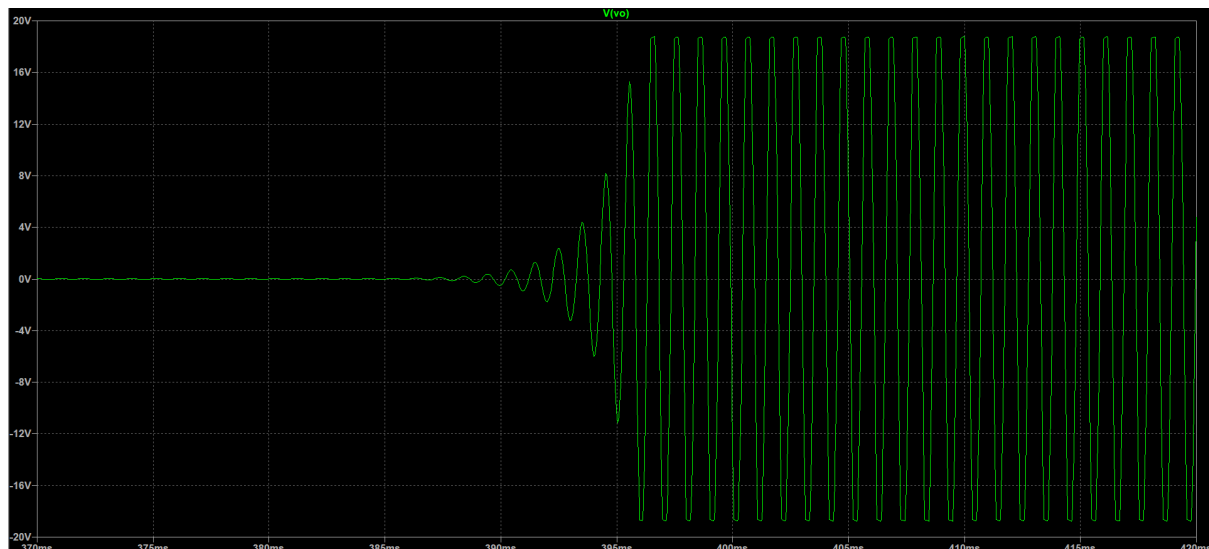


Logarithmic amplifier:


Circuit:

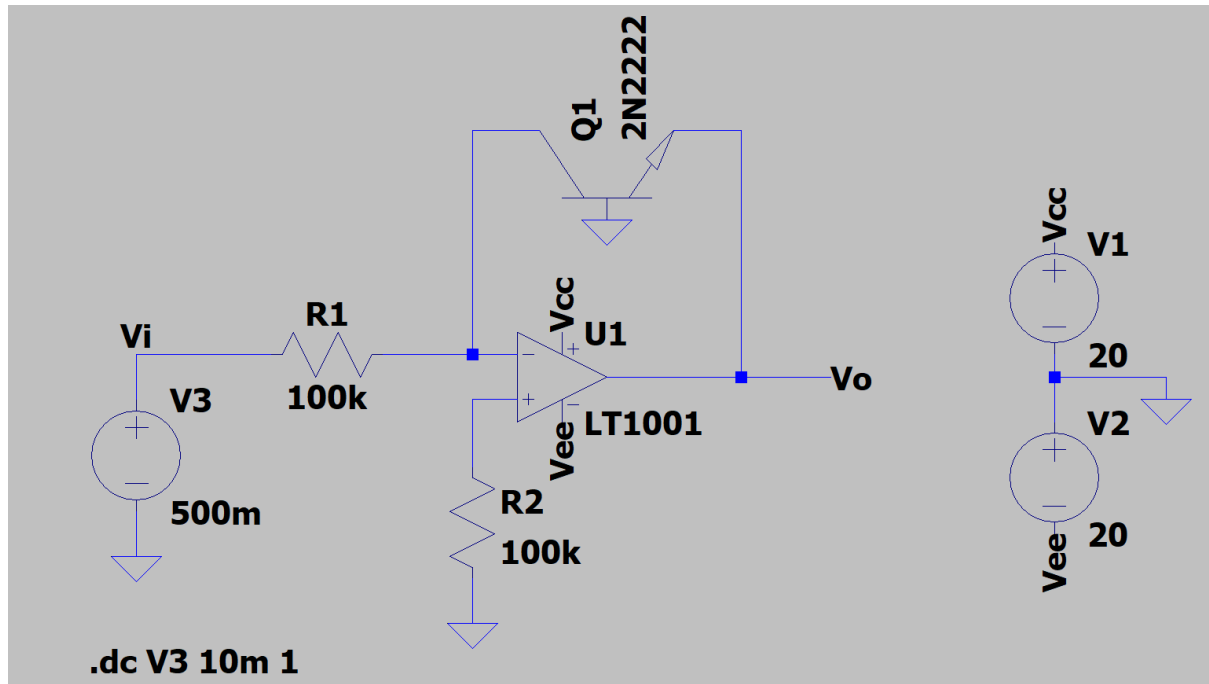

V_o as a function of V_i :

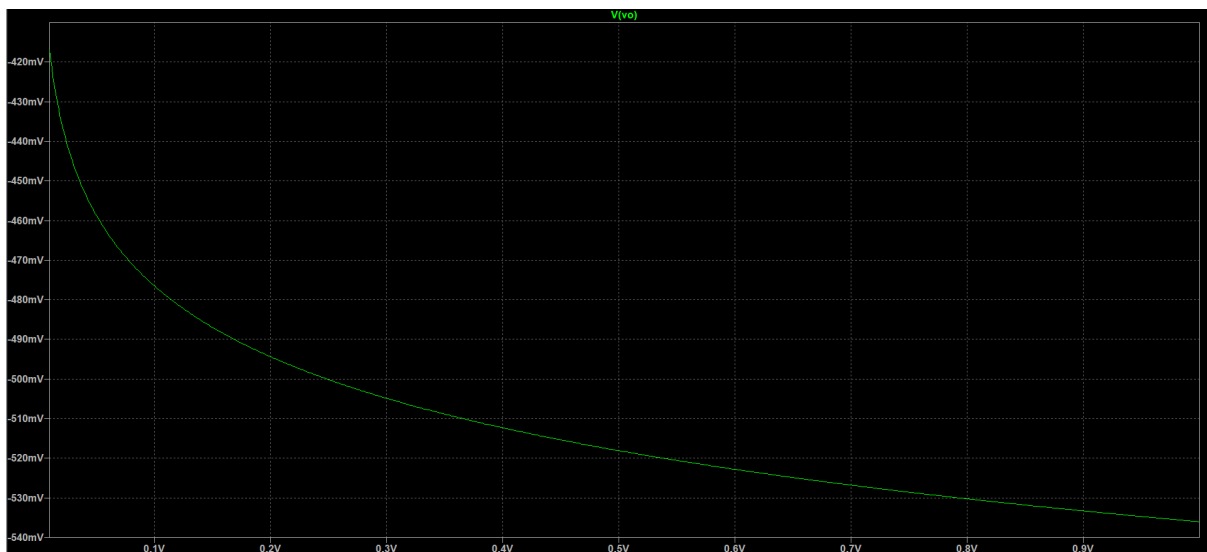


V_o as a function of $\ln(V_i)$:

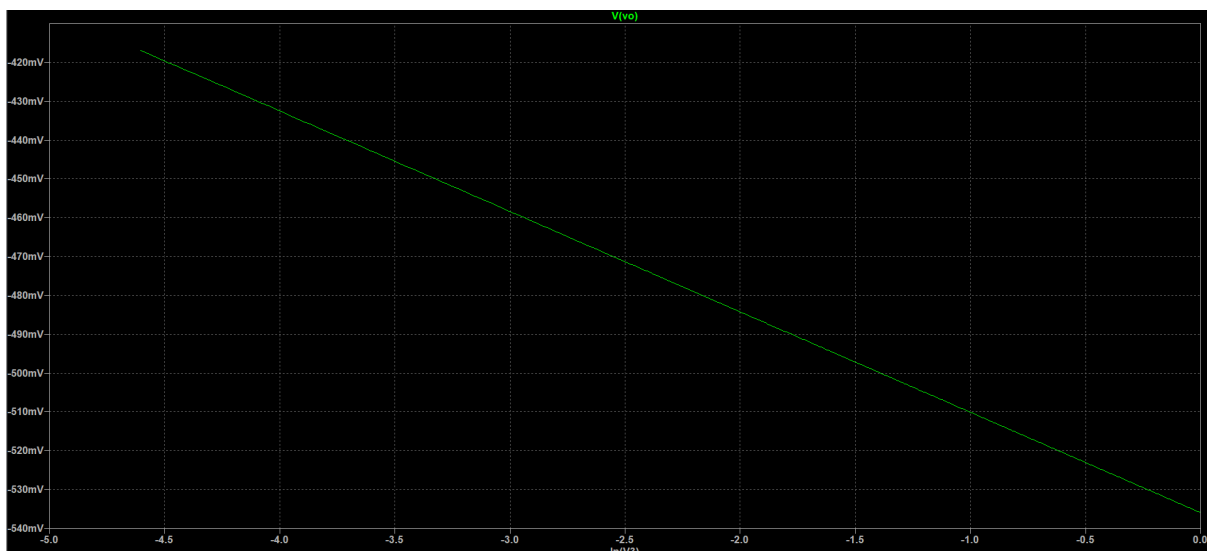


Logarithmic amplifier:

Circuit:

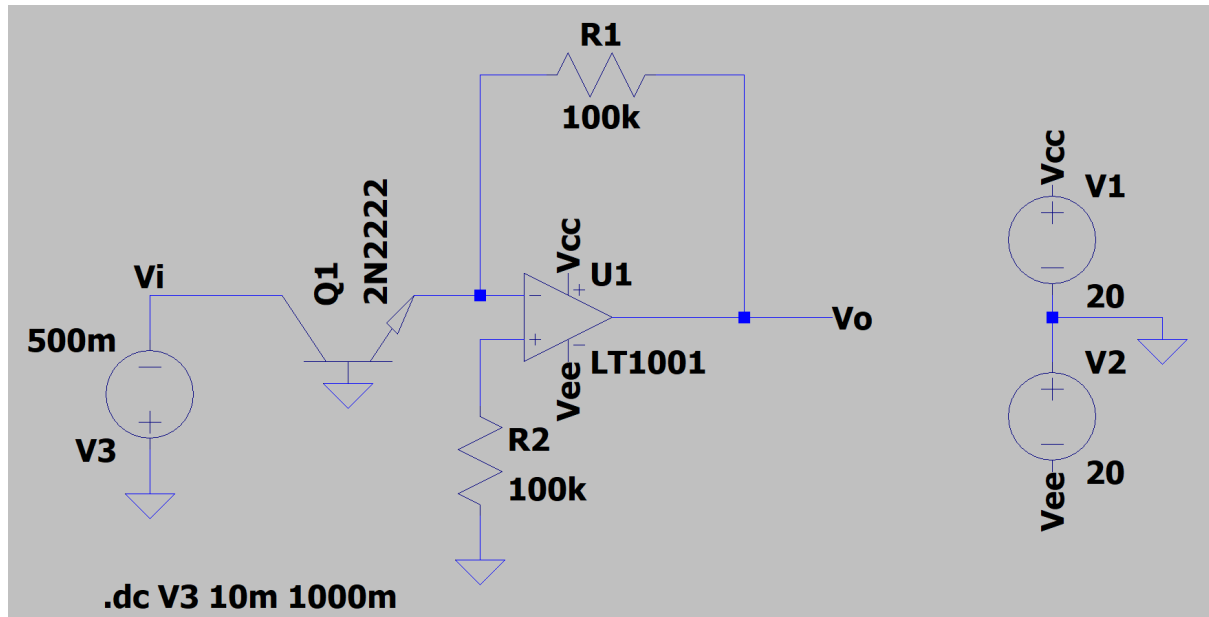

V_o as a function of V_i :

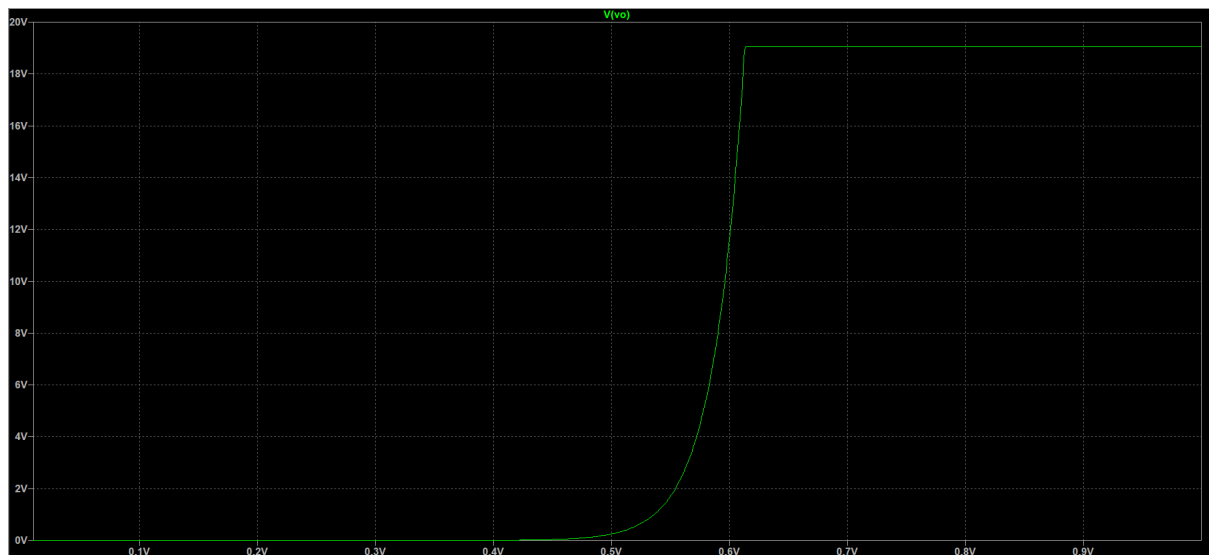

$\ln(V_o)$ as a function of V_i :

